

Chapter 12 Microwave Amplifier Design

12.1 Two-port power gains

power gains G , G_T , G_A

12.2 Stability

input and output stability circles, stability criterion

12.3 Single-stage transistor amplifier design

conjugate match, constant gain circle, noise parameters, constant noise figure circle, LNA (low noise amplifier)


12.4 Broadband transistor amplifier design

balanced amplifier, distributed amplifier, differential amplifier

12.5 Power amplifier

nonlinear operation

12.1 Two-port power gains

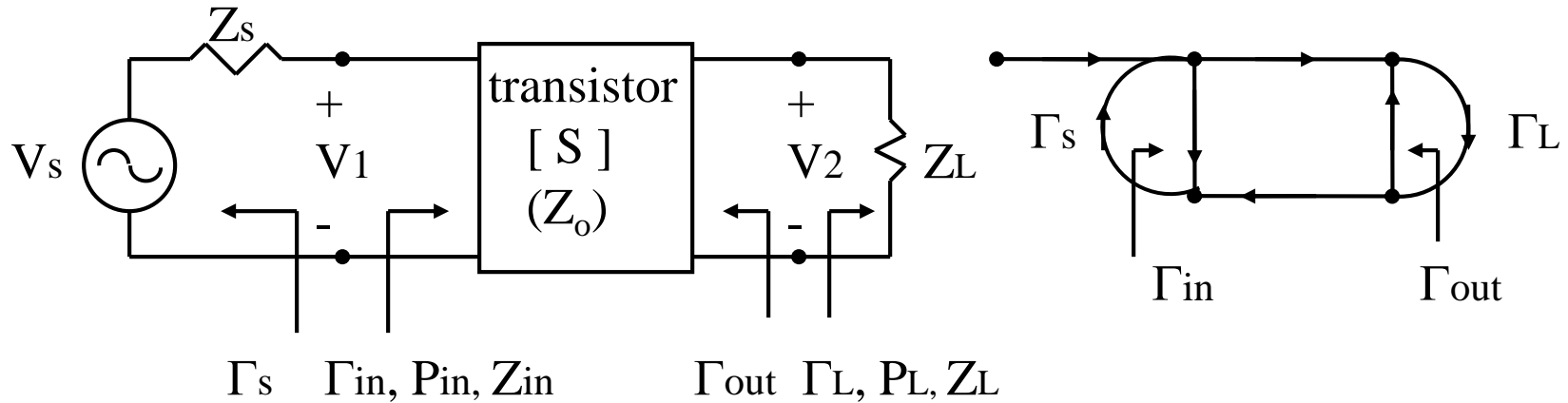

$$\text{power gain } G \equiv \frac{P_L}{P_{in}}(S, \Gamma_L)$$

$$\text{available power gain } G_A \equiv \frac{P_{avn}}{P_{avs}}(S, \Gamma_S)$$

$$\text{transducer power gain } G_T \equiv \frac{P_L}{P_{avs}}(S, \Gamma_S, \Gamma_L)$$

$$P_{in}(\Gamma_{in}), P_{avs}(\Gamma_S) = P_{in}|_{\Gamma_{in}=\Gamma_S^*}, P_L(\Gamma_L), P_{avn}(\Gamma_{out}) = P_L|_{\Gamma_L=\Gamma_{out}^*}$$

Discussion

1.

$$V_1 = V_s \frac{Z_{in}}{Z_s + Z_{in}} = V_1^+ + V_1^- = V_1^+ (1 + \Gamma_{in}),$$

$$\Gamma_{in} = \frac{Z_{in} - Z_o}{Z_{in} + Z_o}, \Gamma_s = \frac{Z_s - Z_o}{Z_s + Z_o}$$

$$\rightarrow V_1^+ = \frac{V_s}{1 + \Gamma_{in}} \frac{Z_{in}}{Z_s + Z_{in}} = \frac{V_s}{2} \frac{1 - \Gamma_s}{1 - \Gamma_s \Gamma_{in}}$$

$$P_{in} = P_s (1 - |\Gamma_{in}|^2) = \frac{1}{2} \frac{|V_1^+|^2}{Z_o} (1 - |\Gamma_{in}|^2) = \frac{|V_s|^2}{8Z_o} \frac{|1 - \Gamma_s|^2}{|1 - \Gamma_s \Gamma_{in}|^2} (1 - |\Gamma_{in}|^2)$$

$$2. V_2^- = S_{21} V_1^+ + S_{22} V_2^+, V_2^+ = \Gamma_L V_2^-, V_1^+ = \frac{V_s}{2} \frac{1 - \Gamma_s}{1 - \Gamma_s \Gamma_{in}}$$

$$\rightarrow V_2^- = \frac{V_s}{2} \frac{S_{21} (1 - \Gamma_s)}{(1 - S_{22} \Gamma_L) (1 - \Gamma_s \Gamma_{in})}$$

$$P_L = P_{out} (1 - |\Gamma_L|^2) = \frac{1}{2} \frac{|V_2^-|^2}{Z_o} (1 - |\Gamma_L|^2) = \frac{|V_s|^2}{8Z_o} \frac{|S_{21}|^2 |1 - \Gamma_s|^2}{|1 - S_{22} \Gamma_L|^2 |1 - \Gamma_s \Gamma_{in}|^2} (1 - |\Gamma_L|^2)$$

$$3. P_{avs} = P_{in} \Big|_{\Gamma_{in}=\Gamma_s^*} = \frac{|V_s|^2}{8Z_o} \frac{|1-\Gamma_s|^2}{1-|\Gamma_s|^2}$$


$$P_{avn} = P_L \Big|_{\Gamma_L=\Gamma_{out}^*} = \frac{|V_s|^2}{8Z_o} \frac{|S_{21}|^2 |1-\Gamma_s|^2 (1-|\Gamma_{out}|^2)}{|1-S_{22}\Gamma_{out}^*|^2 |1-\Gamma_s\Gamma_{in}|^2}, \Gamma_{in} = S_{11} + \frac{S_{12}S_{21}\Gamma_L}{1-S_{22}\Gamma_L}$$

$$\rightarrow P_{avn} = \frac{|V_s|^2}{8Z_o} \frac{|S_{21}|^2 |1-\Gamma_s|^2}{|1-S_{11}\Gamma_s|^2 (1-|\Gamma_{out}|^2)}$$

$$4. G(S, \Gamma_L) \equiv \frac{P_L}{P_{in}} = \frac{|S_{21}|^2 (1-|\Gamma_L|^2)}{(1-|\Gamma_{in}|^2) |1-S_{22}\Gamma_L|^2}$$

$$G_A(S, \Gamma_s) \equiv \frac{P_{avn}}{P_{avs}} = \frac{|S_{21}|^2 (1-|\Gamma_s|^2)}{(1-|\Gamma_{out}|^2) |1-S_{11}\Gamma_s|^2}$$

$$G_T(S, \Gamma_s, \Gamma_L) \equiv \frac{P_L}{P_{avs}} = \frac{|S_{21}|^2 (1-|\Gamma_s|^2)(1-|\Gamma_L|^2)}{|1-\Gamma_s\Gamma_{in}|^2 |1-S_{22}\Gamma_L|^2} (= |S_{21}|^2, \text{ if } \Gamma_s = \Gamma_L = 0)$$

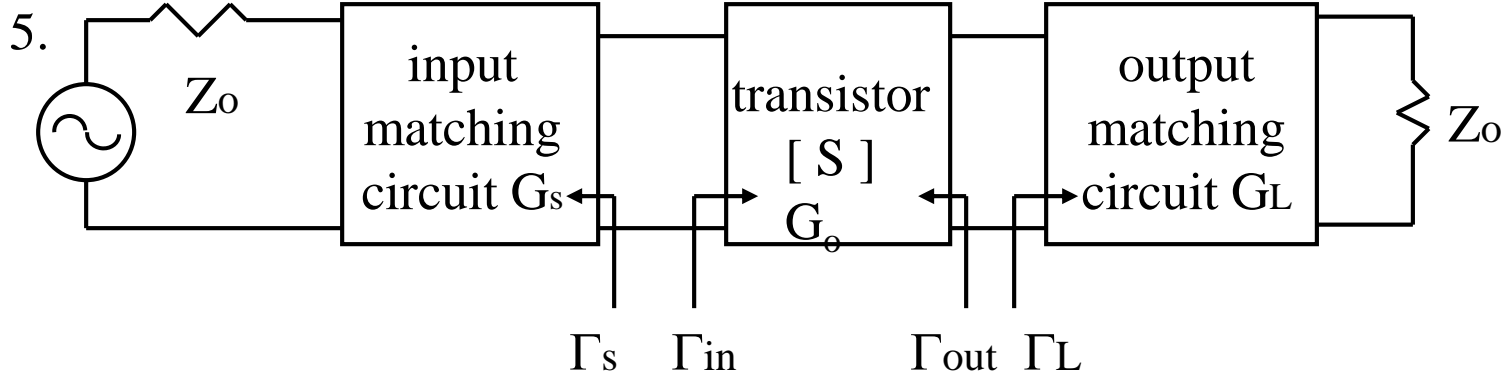

$$G_T = \frac{1 - |\Gamma_s|^2}{|1 - \Gamma_s \Gamma_{in}|^2} |S_{21}|^2 \frac{1 - |\Gamma_L|^2}{|1 - S_{22} \Gamma_L|^2} = G_s G_o G_L$$

$$\Gamma_{in} = \Gamma_s^*, \Gamma_{out} = \Gamma_L^* \rightarrow G_{T \max} = \frac{1}{1 - |\Gamma_s|^2} |S_{21}|^2 \frac{1 - |\Gamma_L|^2}{|1 - S_{22} \Gamma_L|^2}$$

$$S_{12} = 0, \text{ unilateral transducer gain } G_{TU} = \frac{1 - |\Gamma_s|^2}{|1 - S_{11} \Gamma_s|^2} |S_{21}|^2 \frac{1 - |\Gamma_L|^2}{|1 - S_{22} \Gamma_L|^2}$$

$$\Gamma_s = S_{11}^*, \Gamma_L = S_{22}^* \rightarrow G_{TU \max} = \frac{1}{1 - |S_{11}|^2} |S_{21}|^2 \frac{1}{1 - |S_{22}|^2} \Rightarrow \textit{selection of transistor}$$

6. Ex.12.1 A Si BJT@1GHz

$$S_{11} = 0.38 \angle -158^\circ, S_{12} = 0.11 \angle 54^\circ, S_{21} = 3.5 \angle 80^\circ, S_{22} = 0.4 \angle -43^\circ$$

$$Z_s = 25\Omega, Z_L = 40\Omega, Z_o = 50\Omega$$

$$\Gamma_s = \frac{Z_s - Z_o}{Z_s + Z_o} = -0.333, \Gamma_L = \frac{Z_L - Z_o}{Z_L + Z_o} = -0.111$$


$$\Gamma_{in} = S_{11} + \frac{S_{12}S_{21}\Gamma_L}{1 - S_{22}\Gamma_L} = 0.365 \angle -152^\circ$$

$$\Gamma_{out} = S_{22} + \frac{S_{12}S_{21}\Gamma_s}{1 - S_{11}\Gamma_s} = 0.545 \angle -43^\circ$$

$$G = 13.1, G_A = 19.8, G_T = 12.6$$

$$G_T = \frac{P_L}{P_{avs}} < \frac{P_L}{P_{in}} = G, G_A = \frac{P_{avn}}{P_{avs}} < \frac{P_L}{P_{avs}} = G_T$$

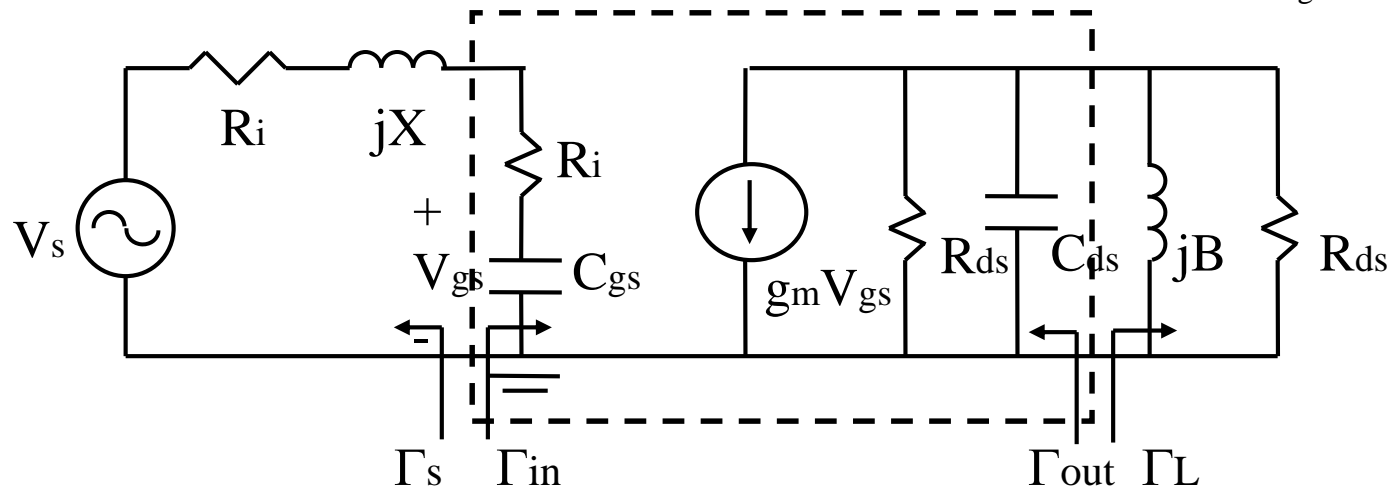7. conjugate match using FET equivalent circuit ($S_{12}=0$, or $C_{gd}=0$)



$$Z_{in} = Z_S^* \rightarrow \frac{1}{\omega C_{gs}} = X, Z_{out} = Z_L^* \rightarrow \omega C_{ds} = -B$$

$$V_{gs} = \frac{V_s}{2R_i} \frac{1}{j\omega C_{gs}}$$

$$G_{TU} = \frac{P_L}{P_{avs}} = \frac{\frac{1}{2} \left(\frac{1}{2} |g_m V_{gs}| \right)^2 R_{ds}}{\frac{1}{2} \left(\frac{1}{2} V_s \right)^2 / R_i} = \frac{g_m^2 R_{ds}}{4\omega^2 R_i C_{gs}^2} = \frac{R_{ds}}{4R_i} \left(\frac{f_T}{f} \right)^2 : 6dB/octave, f_T = \frac{g_m}{2\pi C_{gs}}$$

12.2 Stability (S, f)

unconditional stable $\forall Z_s, Z_L \rightarrow |\Gamma_{in}| < 1, |\Gamma_{out}| < 1$

conditional stable $\exists Z_s, Z_L \rightarrow |\Gamma_{in}| < 1, |\Gamma_{out}| < 1$

Discussion

1. $S_{12} = 0, |\Gamma_{in}| < 1, |\Gamma_{out}| < 1 \rightarrow |S_{11}| < 1, |S_{22}| < 1$

2. $|\Gamma_{in}| = \left| S_{11} + \frac{S_{12}S_{21}\Gamma_L}{1 - S_{22}\Gamma_L} \right| = 1 \rightarrow \text{output stability circle } |\Gamma_L - C_L| = R_L$

$$C_L = \frac{(S_{22} - \Delta S_{11}^*)^*}{|S_{22}|^2 - |\Delta|^2}, R_L = \left| \frac{S_{12}S_{21}}{|S_{22}|^2 - |\Delta|^2} \right|$$

$$|\Gamma_{out}| = \left| S_{22} + \frac{S_{12}S_{21}\Gamma_s}{1 - S_{11}\Gamma_s} \right| = 1 \rightarrow \text{input stability circle } |\Gamma_s - C_s| = R_s$$

$$C_s = \frac{(S_{11} - \Delta S_{22}^*)^*}{|S_{11}|^2 - |\Delta|^2}, R_s = \left| \frac{S_{12}S_{21}}{|S_{11}|^2 - |\Delta|^2} \right|$$


(derivation in p.565)

3. conditional stable

$$|S_{11}| < 1$$

Γ_L -plane


$$|\Gamma_{in}| = 1$$

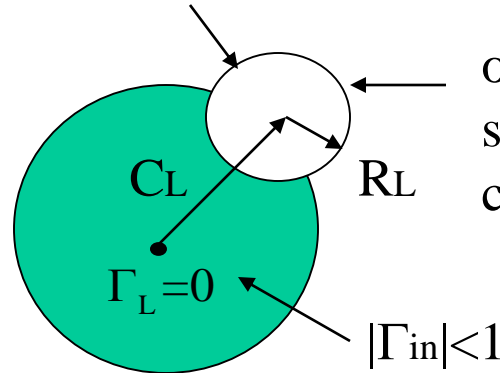

$$|S_{11}| > 1$$

Γ_L -plane


output
stability
circle

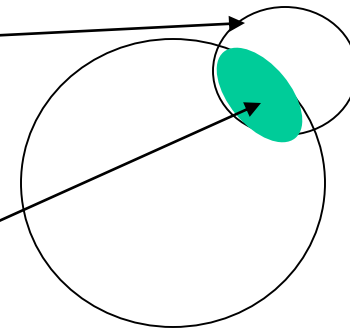

$$|S_{22}| < 1$$

Γ_s -plane


$$|\Gamma_{out}| = 1$$

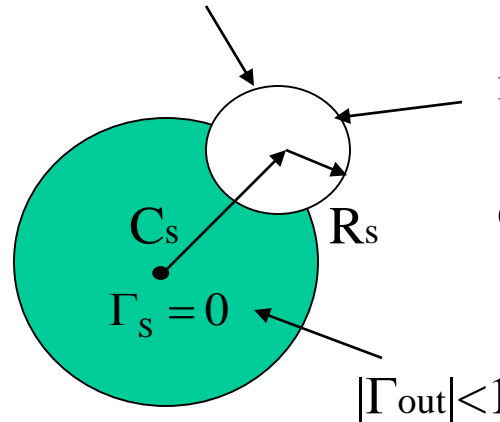

$$|S_{22}| > 1$$


Γ_s -plane

input
stability
circle

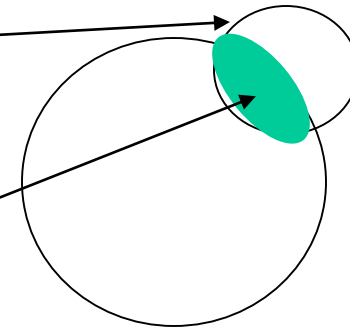


微波電路講義

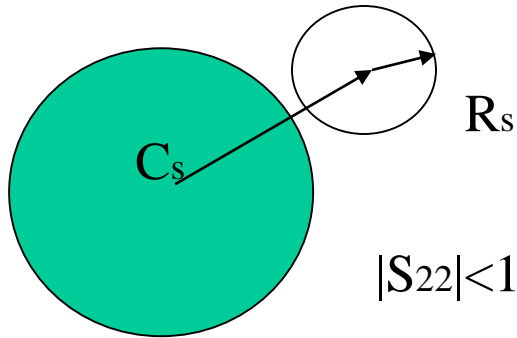4. unconditional stable, stability factor K





$$|S_{22}| < 1$$

$$|C_s - R_s| > 1$$

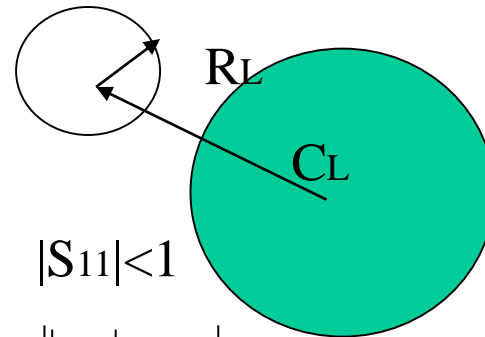

$$|S_{11}| < 1$$

$$|C_L - R_L| > 1$$

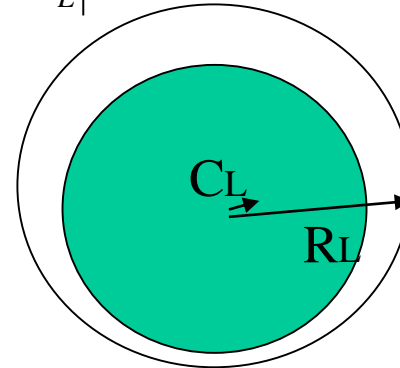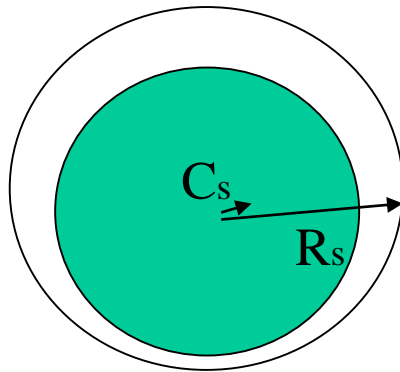

unconditional stable $|S_{11}| < 1, |S_{22}| < 1, |C_s - R_s| > 1, |C_L - R_L| > 1$

$$\Leftrightarrow |\Delta| < 1, K = \frac{1 - |S_{11}|^2 - |S_{22}|^2 + |\Delta|^2}{2|S_{12}S_{21}|} > 1, \Delta = \det[S] : \text{Rollet's condition}$$

(derivation in p.568 and 569)

$\Rightarrow K$, selection of transistor 12-10

5. In practice, one should consider stability over a wide bandwidth for the possible oscillations.

6. Ex.12.2 Triquint T1G6000528 @ 1.9GHz, $Z_o=50\Omega$

$$S_{11} = 0.869 \angle -159^\circ, S_{12} = 0.031 \angle -9^\circ, S_{21} = 4.25 \angle 61^\circ,$$

$$S_{22} = 0.507 \angle -117^\circ$$

$$|\Delta| = 0.336 < 1, K = 0.383 < 1$$

$$\text{input stability circle } C_s = 1.09 \angle 162^\circ, R_s = 0.205$$

$$\text{output stability circle } C_L = 1.59 \angle 132^\circ, R_L = 0.915$$

(p.570, Fig.12.6)

12.3 Single-stage transistor amplifier design

- conjugate match (maximum transducer power gain)

if $|\Delta| < 1$, $K > 1$

→ input and output simultaneously conjugate match $\Gamma_{in} = \Gamma_s^*$, $\Gamma_{out} = \Gamma_L^*$

$$\rightarrow G_T = G_{T_{\max}} = \frac{1}{1 - |\Gamma_s|^2} |S_{21}|^2 \frac{1 - |\Gamma_L|^2}{|1 - S_{22}\Gamma_L|^2} = \left| \frac{S_{21}}{S_{12}} \right| (K - \sqrt{K^2 - 1})$$

$$\Gamma_s^* = \Gamma_{in} = S_{11} + \frac{S_{12}S_{21}\Gamma_L}{1 - S_{22}\Gamma_L} \rightarrow \Gamma_L = \frac{B_2 - \sqrt{B_2^2 - 4|C_2|^2}}{2C_2}$$

$$\Gamma_L^* = \Gamma_{out} = S_{22} + \frac{S_{12}S_{21}\Gamma_s}{1 - S_{11}\Gamma_s} \rightarrow \Gamma_s = \frac{B_1 - \sqrt{B_1^2 - 4|C_1|^2}}{2C_1}$$

$$B_1 = 1 + |S_{11}|^2 - |S_{22}|^2 - |\Delta|^2, B_2 = 1 + |S_{22}|^2 - |S_{11}|^2 - |\Delta|^2$$

$$C_1 = S_{11} - \Delta S_{22}^*, C_2 = S_{22} - \Delta S_{11}^*$$

(derivation in p. 571 and 572)

Discussion

1. linear amplifier design procedure

if $|\Delta| < 1$, $K > 1$ then uses input and output simultaneously conjugate matches for G_{Tmax}

if $K < 1$ then draws input and output stability circles to see if input and output simultaneously conjugate matches possible, otherwise selects proper Γ_s and Γ_L for gain or noise figure considerations.

$$2. S_{12} = 0 \rightarrow \Gamma_s = S_{11}^*, \Gamma_L = S_{22}^*$$


$$G_{TUmax} = \frac{1}{1 - |S_{11}|^2} |S_{21}|^2 \frac{1}{1 - |S_{22}|^2} = G_{smax} |S_{21}|^2 G_{Lmax}$$

3. Ex.12.3 FET @ 4GHz

$$S_{11} = 0.72 \angle -116^\circ, S_{12} = 0.03 \angle 57^\circ, S_{21} = 2.6 \angle 76^\circ, S_{22} = 0.73 \angle -54^\circ$$

$$|\Delta| = 0.488 < 1, K = 1.195 > 1 \rightarrow \Gamma_s = 0.872 \angle 123^\circ, \Gamma_L = 0.876 \angle 61^\circ$$


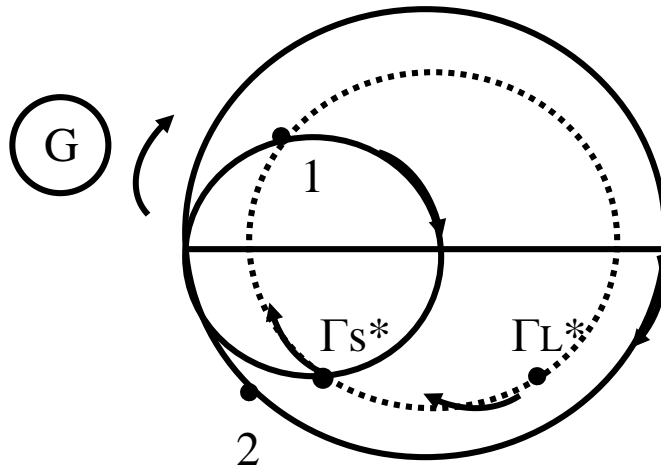
$$G_{Tmax} = 6.2 + 8.3 + 2.22 = 16.7 \text{ dB}$$



$$\Gamma_s^* = 0.872 \angle -123^\circ$$

$$\Gamma_L^* = 0.876 \angle -61^\circ$$

1. $y = 1 - j3.5$
2. $y = j3.5$

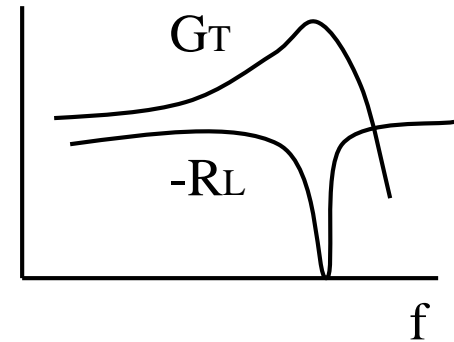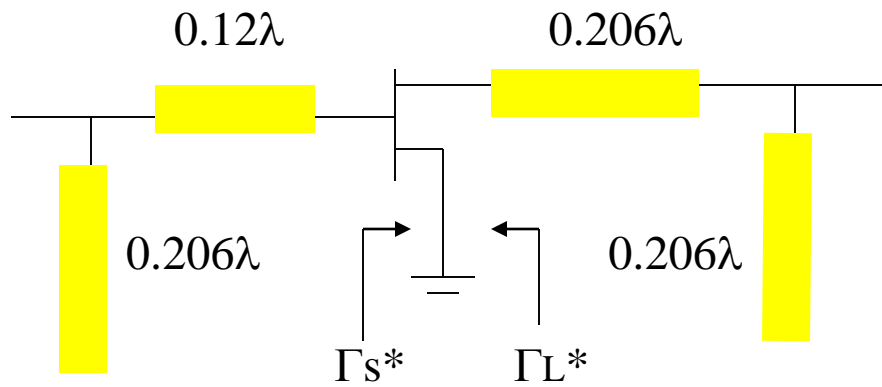

frequency response (p.575, Fig.12.7)

- constant gain circle ($S_{12}=0$, unilateral assumption)

$$G_T = \frac{1 - |\Gamma_s|^2}{|1 - \Gamma_s \Gamma_{in}|^2} |S_{21}|^2 \frac{1 - |\Gamma_L|^2}{|1 - S_{22} \Gamma_L|^2}, S_{12} = 0 \rightarrow \Gamma_{in} = S_{11}$$

$$G_s = \frac{1 - |\Gamma_s|^2}{|1 - S_{11} \Gamma_s|^2}, G_{s \max} = \frac{1}{1 - |S_{11}|^2}, G_L = \frac{1 - |\Gamma_L|^2}{|1 - S_{22} \Gamma_L|^2}, G_{L \max} = \frac{1}{1 - |S_{22}|^2}$$

$$g_s \equiv \frac{G_s}{G_{s \max}} \rightarrow \text{constant gain circle in } \Gamma_s \text{-plane } |\Gamma_s - C_s| = R_s$$

$$g_L \equiv \frac{G_L}{G_{L \max}} \rightarrow \text{constant gain circle in } \Gamma_L \text{-plane } |\Gamma_L - C_L| = R_L$$

$$C_s = \frac{g_s S_{11}^*}{1 - (1 - g_s) |S_{11}|^2}, R_s = \frac{\sqrt{1 - g_s} (1 - |S_{11}|^2)}{1 - (1 - g_s) |S_{11}|^2}$$

$$C_L = \frac{g_L S_{22}^*}{1 - (1 - g_L) |S_{22}|^2}, R_L = \frac{\sqrt{1 - g_L} (1 - |S_{22}|^2)}{1 - (1 - g_L) |S_{22}|^2}$$

(derivation in p. 576 and 577)

Discussion

1. $G_s=0\text{dB}$ and $G_L=0\text{dB}$ circles pass through the Smith chart center.

$$G_s = \frac{1-|\Gamma_s|^2}{|1-S_{11}\Gamma_s|^2} (=0\text{dB}) = 1, G_{s\max} = \frac{1}{1-|S_{11}|^2},$$

$$G_L = \frac{1-|\Gamma_L|^2}{|1-S_{22}\Gamma_L|^2} (=0\text{dB}) = 1, G_{L\max} = \frac{1}{1-|S_{22}|^2}$$

$$g_s = \frac{G_s}{G_{s\max}} = \frac{1}{G_{s\max}} = 1-|S_{11}|^2 \rightarrow 1-g_s = |S_{11}|^2,$$


$$g_L = \frac{G_L}{G_{L\max}} = \frac{1}{G_{L\max}} = 1-|S_{22}|^2 \rightarrow 1-g_L = |S_{22}|^2$$

constant gain circles $|\Gamma_s - C_s| = R_s, |\Gamma_L - C_L| = R_L$

$$C_s = \frac{g_s S_{11}^*}{1-(1-g_s)|S_{11}|^2} = \frac{(1-|S_{11}|^2)S_{11}^*}{1-|S_{11}|^4} = \frac{S_{11}^*}{1+|S_{11}|^2}, R_s = \frac{\sqrt{1-g_s}(1-|S_{11}|^2)}{1-(1-g_s)|S_{11}|^2} = \frac{|S_{11}|(1-|S_{11}|^2)}{1-|S_{11}|^4} = \frac{|S_{11}|}{1+|S_{11}|^2}$$

$$C_L = \frac{g_L S_{22}^*}{1-(1-g_L)|S_{22}|^2} = \frac{(1-|S_{22}|^2)S_{22}^*}{1-|S_{22}|^4} = \frac{S_{22}^*}{1+|S_{22}|^2}, R_L = \frac{\sqrt{1-g_L}(1-|S_{22}|^2)}{1-(1-g_L)|S_{22}|^2} = \frac{|S_{22}|(1-|S_{22}|^2)}{1-|S_{22}|^4} = \frac{|S_{22}|}{1+|S_{22}|^2}$$

$$\rightarrow |C_s| = R_s, |C_L| = R_L \rightarrow \Gamma_s = \Gamma_L = 0$$

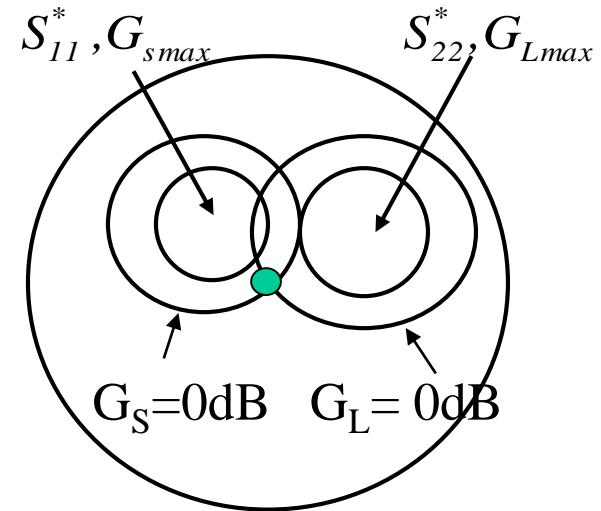


2. Centers of constant gain circles are distributed along the lines from S_{11}^* and S_{22}^* to the Smith chart center, respectively.

$$C_s = \frac{g_s S_{11}^*}{1 - (1 - g_s) |S_{11}|^2}, C_L = \frac{g_L S_{22}^*}{1 - (1 - g_L) |S_{22}|^2}$$

$$g_s = 1, g_L = 1 \rightarrow C_{s,1} = S_{11}^*, C_{L,1} = S_{22}^*$$

$$G_s = 1, G_L = 1 \rightarrow C_{s,2} = \frac{S_{11}^*}{1 + |S_{11}|^2}, C_{L,2} = \frac{S_{22}^*}{1 + |S_{22}|^2}$$
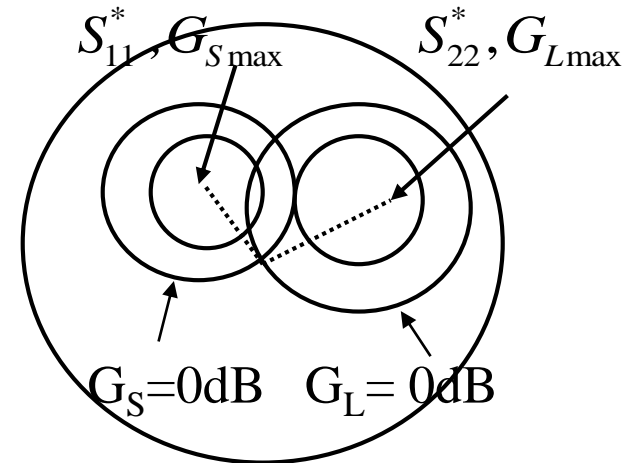
$$\Rightarrow \tan^{-1} \frac{\text{Re}(C_{s,1})}{\text{Im}(C_{s,1})} = \tan^{-1} \frac{\text{Re}(C_{s,2})}{\text{Im}(C_{s,2})}, \tan^{-1} \frac{\text{Re}(C_{L,1})}{\text{Im}(C_{L,1})} = \tan^{-1} \frac{\text{Re}(C_{L,2})}{\text{Im}(C_{L,2})}$$



$$2. \quad \frac{1}{(1+U)^2} < \frac{G_T}{G_{TU}} < \frac{1}{(1-U)^2}$$


$$U = \frac{|S_{11}| |S_{21}| |S_{12}| |S_{22}|}{(1 - |S_{11}|^2)(1 - |S_{22}|^2)} \quad \text{unilateral figure of merit}$$

3. Ex.12.4 design an amplifier with $G_T=11\text{dB}$ @ 4GHz

$$S_{11} = 0.75 \angle -120^\circ, S_{12} = 0, S_{21} = 2.5 \angle 80^\circ, S_{22} = 0.6 \angle -70^\circ$$



$$G_{TU \max} = 3.6 + 8 + 1.9 = 13.5 \text{ dB}$$
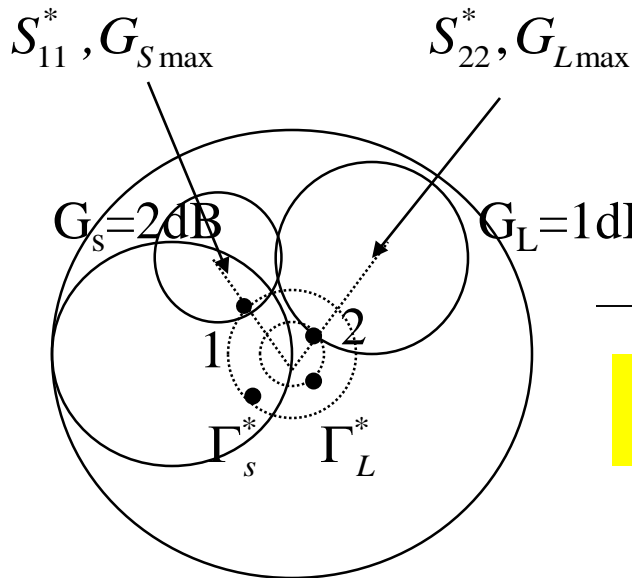
$$\text{choose } G_{TU} = 2 + 8 + 1 = 11 \text{ dB}$$



$$1. \Gamma_s = 0.33 \angle 120^\circ, \Gamma_s^* = 0.33 \angle -120^\circ$$
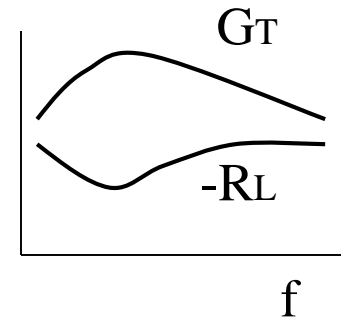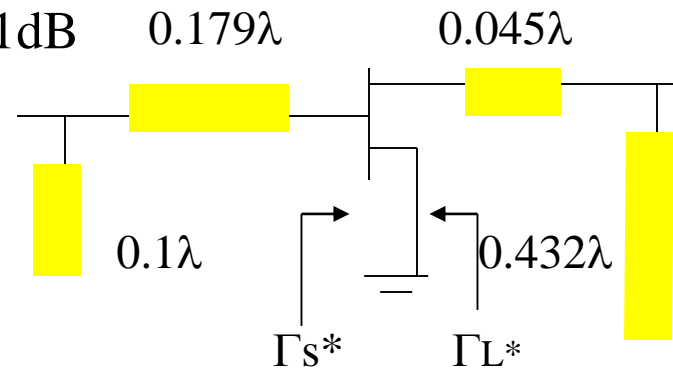
$$2. \Gamma_L = 0.22 \angle 70^\circ, \Gamma_L^* = 0.22 \angle -70^\circ$$



frequency response (p.579, Fig.12.8)

- constant noise figure circle
for a two-port amplifier

$$F = F_{\min} + \frac{R_N}{G_s} |Y_s - Y_{opt}|^2 = F_{\min} + \frac{4R_N}{Z_o} \frac{|\Gamma_s - \Gamma_{opt}|^2}{(1 - |\Gamma_s|^2) |1 + \Gamma_{opt}|^2}$$

noise parameter: F_{\min}, Y_{opt}, R_N equivalent noise resistance of transistor

$$N \equiv \frac{|\Gamma_s - \Gamma_{opt}|^2}{1 - |\Gamma_s|^2} = \frac{F - F_{\min}}{4R_N / Z_o} |1 + \Gamma_{opt}|^2$$

→ constant noise figure circle $|\Gamma_s - C_F| = R_F$

$$C_F = \frac{\Gamma_{opt}}{N+1}, R_F = \frac{\sqrt{N(N+1 - |\Gamma_{opt}|^2)}}{N+1}$$

(derivation in p. 580 and 581)

Discussion

1. Ex.12.5 design a LNA with $F=2\text{dB}$ and max. gain @ 4GHz

$$S_{11} = 0.6\angle -60^\circ, S_{12} = 0.05\angle 26^\circ, S_{21} = 1.9\angle 81^\circ, S_{22} = 0.5\angle -60^\circ$$

$$F_{\min} = 1.6\text{dB}, \Gamma_{opt} = 0.62\angle 100^\circ, R_N = 20\Omega$$



$$U = 0.059$$

$$0.89 = \frac{1}{(1+U)^2} < \frac{G_T}{G_{TU}} < \frac{1}{(1-U)^2} = 1.13, -0.5\text{dB} < G_T - G_{TU} < 0.53\text{dB}$$


$$F = 2\text{dB} \rightarrow C_F = 0.56\angle 100^\circ, R_F = 0.24$$

$$G_s = 1.7\text{dB} \rightarrow C_s = 0.58\angle 60^\circ, R_s = 0.15 \rightarrow \Gamma_s = 0.53\angle 75^\circ$$

$$\Gamma_L = S_{22}^* = 0.5\angle 60^\circ \rightarrow G_L = \frac{1}{1-|S_{22}|^2} = 1.25\text{dB} \rightarrow G_{TU} = 1.7 + |S_{21}|^2 + 1.25 = 8.53\text{dB}$$

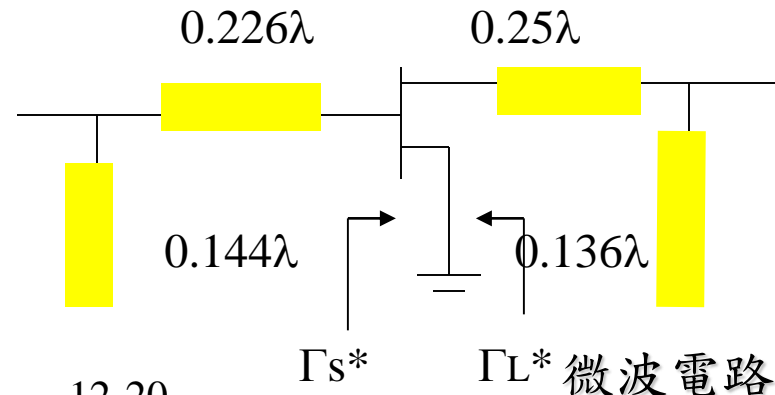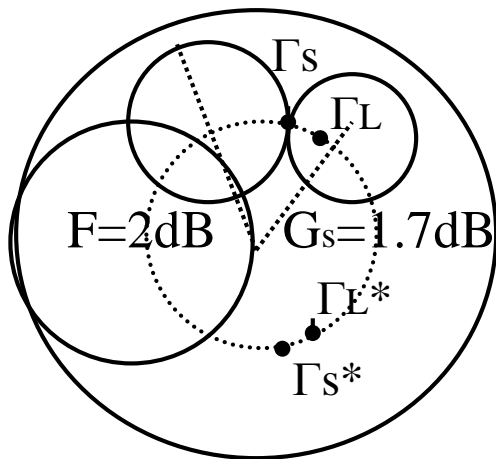


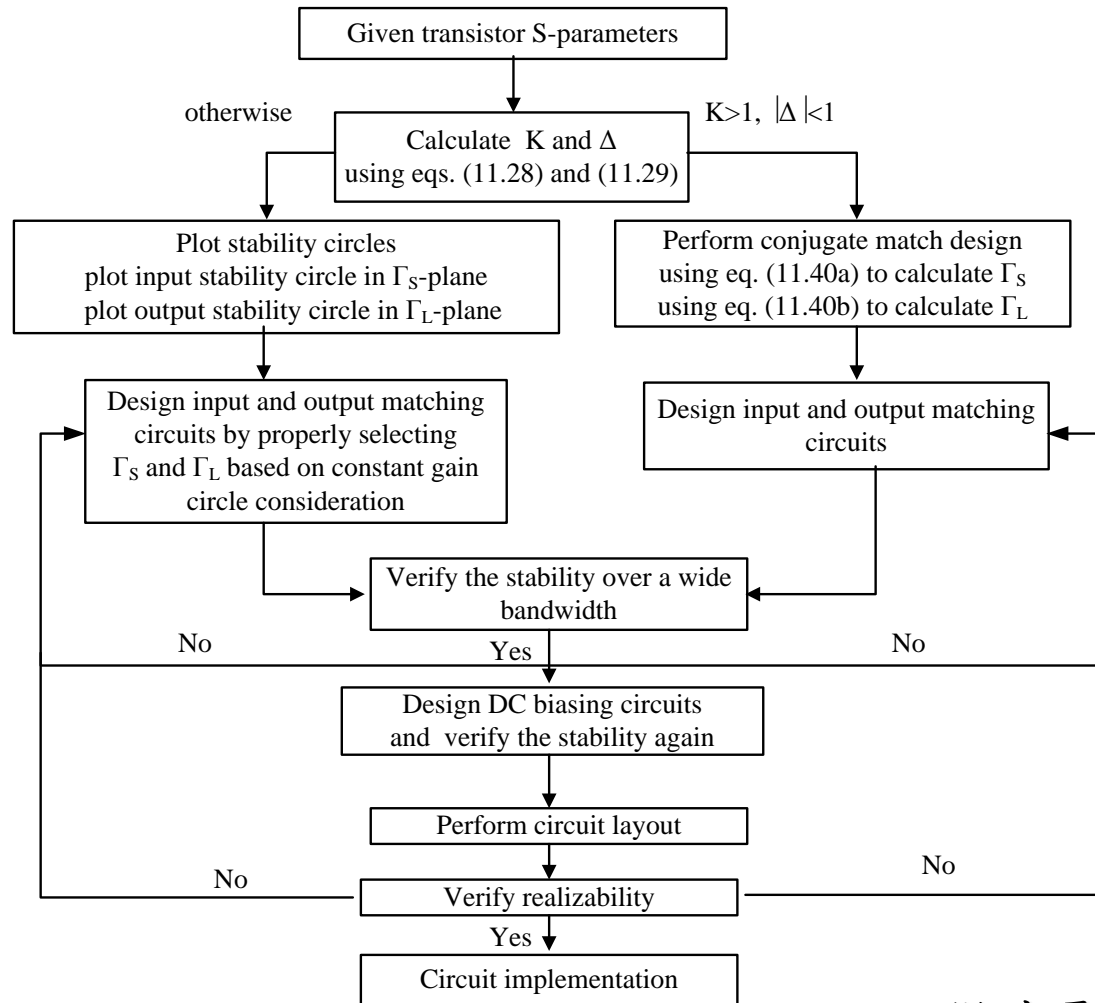2. Approach for single-stage linear amplifier design




3. Two approaches for multi-stage amplifier design

(1)

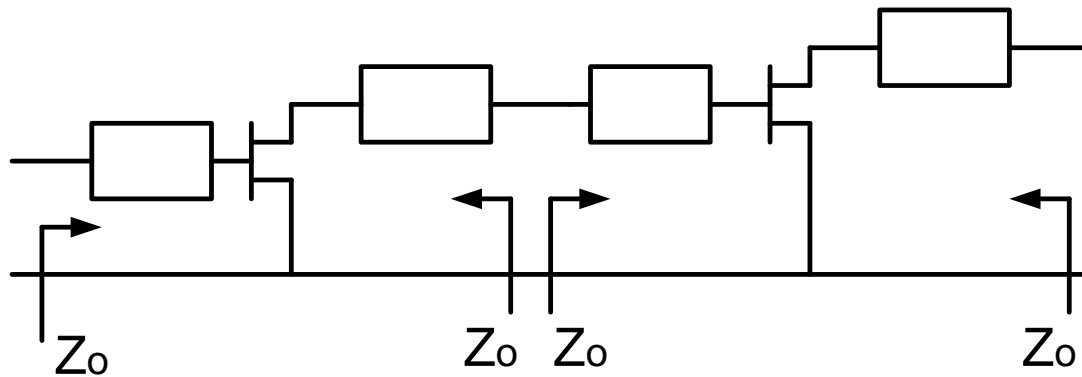


(2)

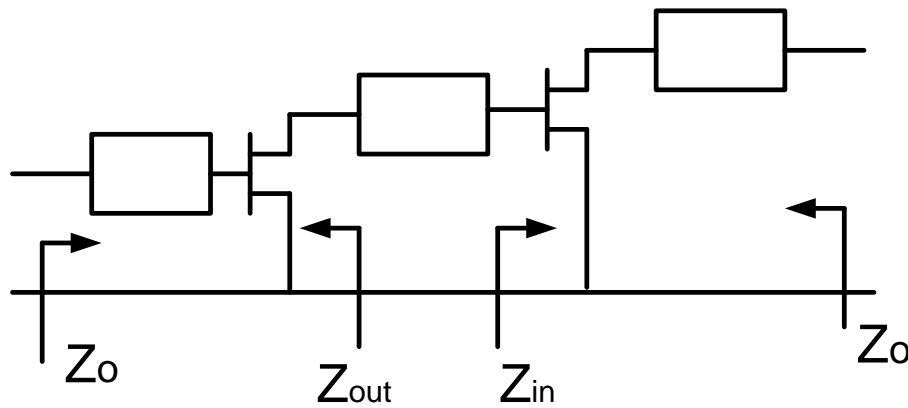

12.4 Broadband transistor amplifier design

- Balanced amplifier

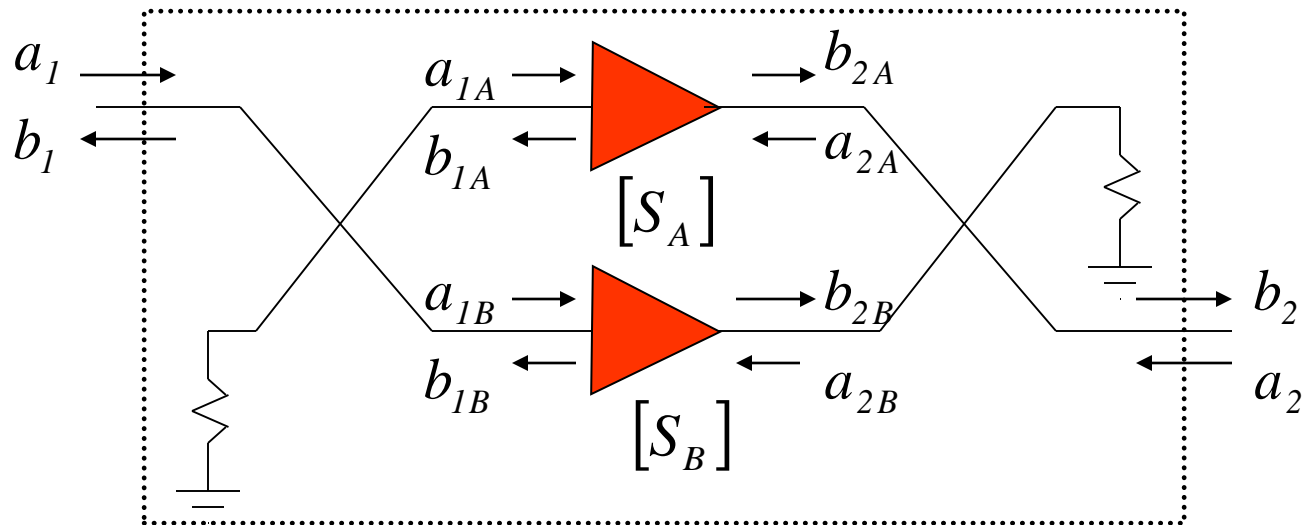



$$\begin{bmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{bmatrix} = \frac{1}{2} \begin{bmatrix} S_{11A} - S_{11B} & -j(S_{12A} + S_{12B}) \\ -j(S_{21A} + S_{21B}) & -(S_{22A} - S_{22B}) \end{bmatrix}$$

Discussion

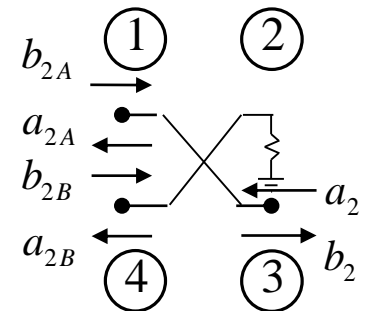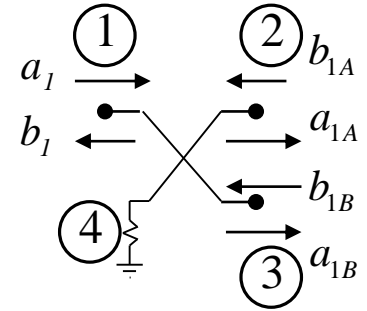1. Derivation of S-parameters

$$90^\circ \text{ hybrid} \begin{bmatrix} 0 & \frac{1}{\sqrt{2}} & \frac{-j}{\sqrt{2}} & 0 \\ \frac{1}{\sqrt{2}} & 0 & 0 & \frac{-j}{\sqrt{2}} \\ \frac{-j}{\sqrt{2}} & 0 & 0 & \frac{1}{\sqrt{2}} \\ 0 & \frac{-j}{\sqrt{2}} & \frac{1}{\sqrt{2}} & 0 \end{bmatrix}, \begin{bmatrix} b_1 \\ a_{1A} \\ a_{1B} \\ - \end{bmatrix} = \begin{bmatrix} 0 & \frac{1}{\sqrt{2}} & \frac{-j}{\sqrt{2}} & 0 \\ \frac{1}{\sqrt{2}} & 0 & 0 & \frac{-j}{\sqrt{2}} \\ \frac{-j}{\sqrt{2}} & 0 & 0 & \frac{1}{\sqrt{2}} \\ 0 & \frac{-j}{\sqrt{2}} & \frac{1}{\sqrt{2}} & 0 \end{bmatrix} \begin{bmatrix} a_1 \\ b_{1A} \\ b_{1B} \\ 0 \end{bmatrix}$$

$$\begin{bmatrix} b_{1A,B} \\ b_{2A,B} \end{bmatrix} = \begin{bmatrix} S_{11A,B} & S_{12A,B} \\ S_{21A,B} & S_{22A,B} \end{bmatrix} \begin{bmatrix} a_{1A,B} \\ a_{2A,B} \end{bmatrix}, \begin{bmatrix} a_{2A} \\ - \\ b_2 \\ a_{2B} \end{bmatrix} = \begin{bmatrix} 0 & \frac{1}{\sqrt{2}} & \frac{-j}{\sqrt{2}} & 0 \\ \frac{1}{\sqrt{2}} & 0 & 0 & \frac{-j}{\sqrt{2}} \\ \frac{-j}{\sqrt{2}} & 0 & 0 & \frac{1}{\sqrt{2}} \\ 0 & \frac{-j}{\sqrt{2}} & \frac{1}{\sqrt{2}} & 0 \end{bmatrix} \begin{bmatrix} b_{2A} \\ 0 \\ a_2 \\ b_{2B} \end{bmatrix}$$



$$\begin{aligned}
b_1 &= \frac{1}{\sqrt{2}} b_{1A} + \frac{-j}{\sqrt{2}} b_{1B} \\
&= \frac{1}{\sqrt{2}} (S_{11A} a_{1A} + S_{12A} a_{2A}) + \frac{-j}{\sqrt{2}} (S_{11B} a_{1B} + S_{12B} a_{2B}) \\
&= \frac{1}{\sqrt{2}} (S_{11A} \frac{1}{\sqrt{2}} a_1 + S_{12A} \frac{-j}{\sqrt{2}} a_2) + \frac{-j}{\sqrt{2}} (S_{11B} \frac{-j}{\sqrt{2}} a_1 + S_{12B} \frac{1}{\sqrt{2}} a_2) \\
&= \frac{1}{2} (S_{11A} - S_{11B}) a_1 + \frac{-j}{2} (S_{12A} + S_{12B}) a_2
\end{aligned}$$


$$\begin{aligned}
b_2 &= \frac{-j}{\sqrt{2}} b_{2A} + \frac{1}{\sqrt{2}} b_{2B} \\
&= \frac{-j}{\sqrt{2}} (S_{21A} a_{1A} + S_{22A} a_{2A}) + \frac{1}{\sqrt{2}} (S_{21B} a_{1B} + S_{22B} a_{2B}) \\
&= \frac{-j}{\sqrt{2}} (S_{21A} \frac{1}{\sqrt{2}} a_1 + S_{22A} \frac{-j}{\sqrt{2}} a_2) + \frac{1}{\sqrt{2}} (S_{21B} \frac{-j}{\sqrt{2}} a_1 + S_{22B} \frac{1}{\sqrt{2}} a_2) \\
&= \frac{-j}{2} (S_{21A} + S_{21B}) a_1 + \frac{-1}{2} (S_{22A} - S_{22B}) a_2
\end{aligned}$$

2. amplifier A=amplifier B, good i/p and o/p match
→ good stability

$$\begin{bmatrix} 0 & -jS_{12A} \\ -jS_{21A} & 0 \end{bmatrix}$$

3. high reliability and less tuning work
4. I/p and o/p matching are improved by two 90° hybrids, and mismatch reflections are absorbed by two resistors.
5. If one transistors fails, gain drops 6dB.
→ graceful degradation
6. disadvantages: larger size and lower efficiency
7. Bandwidth is limited by two hybrids.

8. Power amplifier application

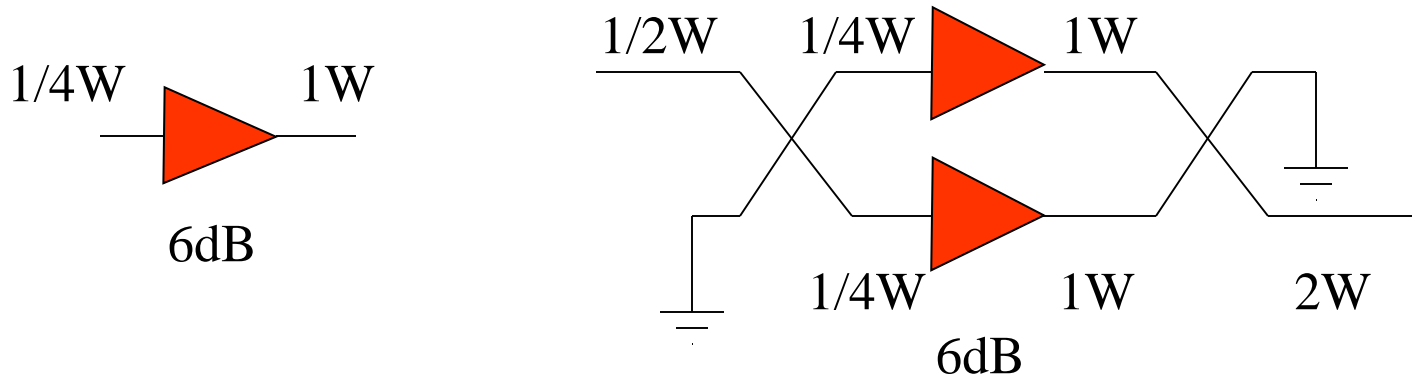


9. Balanced amplifiers can be implemented in a tree structure with a very high power in radar and communication applications.
10. Ex 12.7, two amplifiers of ex.12.4 are implemented as a balanced amplifier to improve its i/p and o/p return loss at 4 GHz. Then, the stub lengths are optimize to give better matching and gain flatness from 3 to 5 GHz bandwidth.
frequency response (p.588, Fig.12.11)

- Distributed (traveling wave) amplifier



TEM line “extreme wide operation bandwidth”


cut off frequency

$$f_c = \frac{1}{\pi\sqrt{LC}}$$

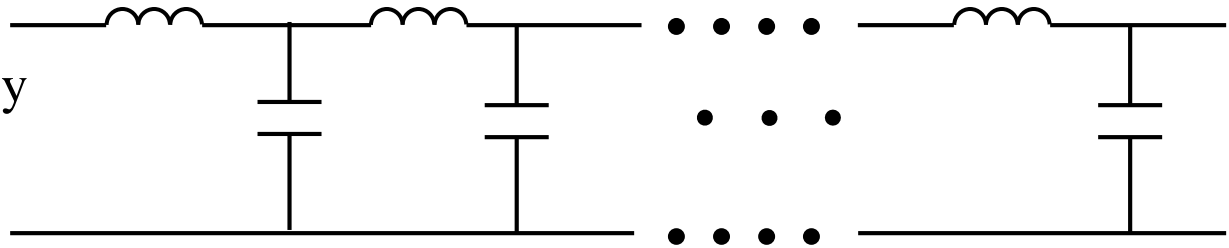


FET equivalent circuit

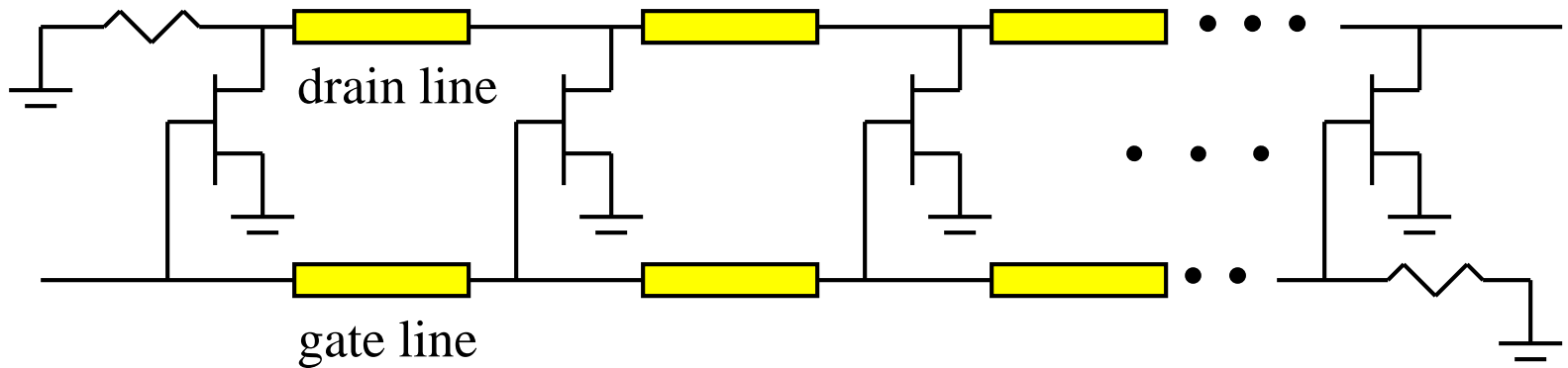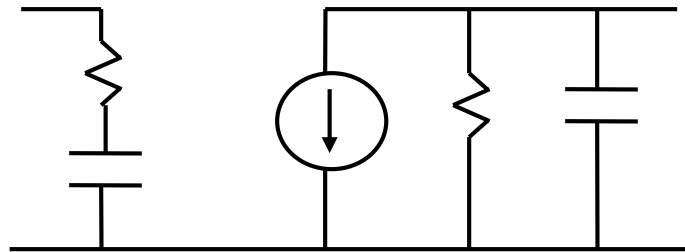

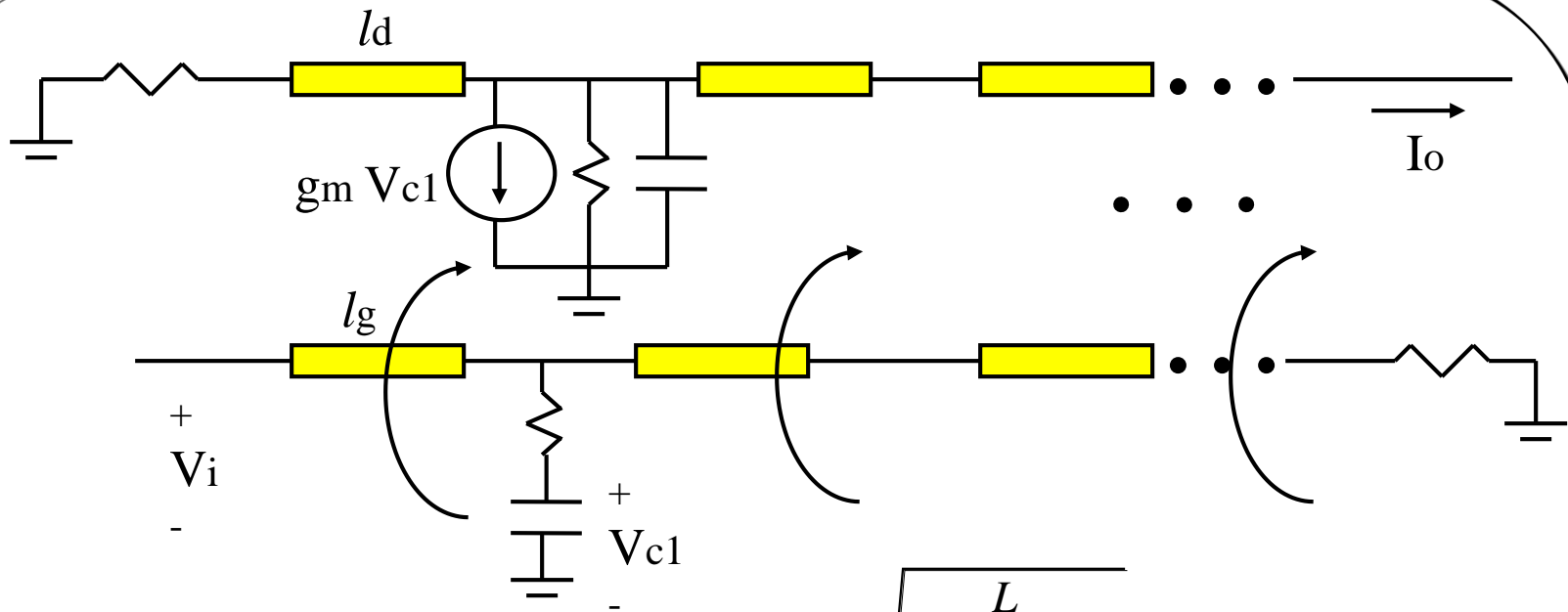

Discussion

1. unit cell of gate line

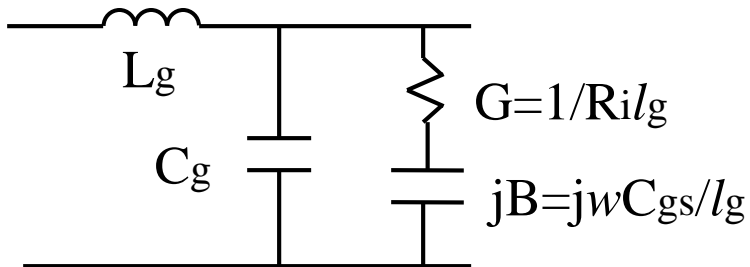

$$G = 1/R_i l_g$$

$$jB = j\omega C_{gs} / l_g$$

$$Z_g \approx \sqrt{\frac{L_g}{C_g + C_{gs} / l_g}}$$

$$\gamma_g = \sqrt{j\omega L_g \left(j\omega C_g + \frac{j\omega C_{gs} / l_g}{1 + j\omega R_i C_{gs}} \right)}$$

$$\underset{\substack{\text{small loss} \\ \omega R_i C_{gs} \ll 1}}{\approx} \frac{\omega^2 R_i Z_g C_{gs}^2}{2l_g} + j\omega \sqrt{L_g \left(C_g + \frac{C_{gs}}{l_g} \right)}$$

$$= \alpha_g + j\beta_g$$

(derivation of 1)

$$Z = j\omega L_g, Y = j\omega C_g + \frac{j\omega C_{gs} / l_g}{1 + j\omega R_i C_{gs}}$$


$$Z_g = \sqrt{\frac{Z}{Y}} \stackrel{\text{small loss}}{\approx} \sqrt{\frac{L_g}{C_g + C_{gs} / l_g}} \quad \text{w}R_i C_{gs} \ll 1$$

$$\gamma_g = \sqrt{ZY} = \sqrt{j\omega L_g \left(j\omega C_g + \frac{j\omega C_{gs} / l_g}{1 + j\omega R_i C_{gs}} \right)} \stackrel{\text{w}R_i C_{gs} \ll 1}{\approx} \sqrt{j\omega L_g \left[j\omega C_g + \frac{j\omega C_{gs} (1 - j\omega R_i C_{gs})}{l_g} \right]}$$


$$= \sqrt{(j\omega)^2 L_g \left(C_g + \frac{C_{gs}}{l_g} \right) - \frac{(j\omega)^3 L_g R_i C_{gs}^2}{l_g}}$$

$$\stackrel{(a-b)^2 \approx a^2 - 2ab}{\approx} \sqrt{(j\omega)^2 L_g \left(C_g + \frac{C_{gs}}{l_g} \right) - \frac{1}{2} \frac{(j\omega)^3 L_g R_i C_{gs}^2 / l_g}{j\omega \sqrt{L_g \left(C_g + \frac{C_{gs}}{l_g} \right)}}$$
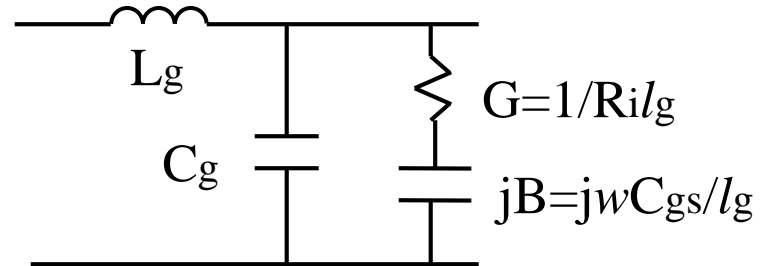
$$= j\omega \sqrt{L_g \left(C_g + \frac{C_{gs}}{l_g} \right)} + \frac{\omega^2}{2} \sqrt{\frac{L_g}{C_g + \frac{C_{gs}}{l_g}}} \frac{R_i C_{gs}^2}{l_g} = j\omega \sqrt{L_g \left(C_g + \frac{C_{gs}}{l_g} \right)} + \frac{\omega^2 R_i C_{gs}^2 Z_g}{2l_g} = \alpha_g + j\beta_g$$



2. unit cell of drain line

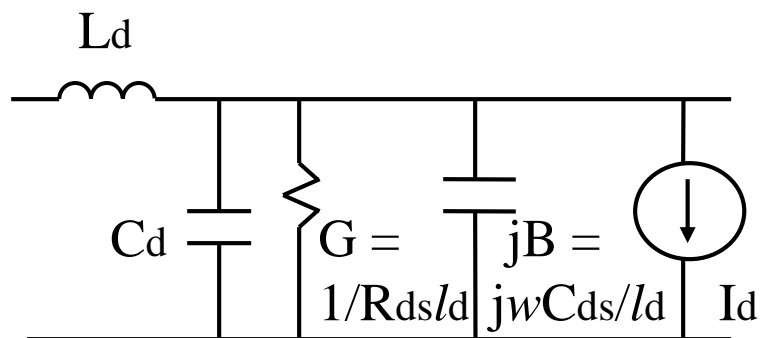

$$Z_d \approx \sqrt{\frac{L_d}{C_d + C_{ds}/l_d}}$$

$$\gamma_d = \sqrt{j\omega L_d \left[\frac{1}{R_{ds}l_d} + j\omega \left(C_d + \frac{C_{ds}}{l_d} \right) \right]}$$

$$\text{small loss} \approx \frac{Z_d}{2R_{ds}l_d} + j\omega \sqrt{L_d \left(C_d + \frac{C_{ds}}{l_d} \right)}$$

$$= \alpha_d + j\beta_d$$

3. o/p current

$$I_o = -\frac{1}{2} \sum_{n=1}^N I_{dn} e^{-(N-n)\gamma_d l_d}, I_{dn} = g_m V_{cn}, V_{cn} = V_i e^{-(n-1)\gamma_g l_g} \left(\frac{1}{1 + j\omega R_i C_{gs}} \right)$$

$$\rightarrow I_o = -\frac{g_m V_i}{2} e^{-N\gamma_d l_d} e^{\gamma_g l_g} \sum_{n=1}^N e^{-n(\gamma_g l_g - \gamma_d l_d)} = -\frac{g_m V_i}{2} \frac{e^{-N\gamma_g l_g} - e^{-N\gamma_d l_d}}{e^{-\gamma_g l_g} - e^{-\gamma_d l_d}}$$

(derivation of 2)

$$Z = j\omega L_d, Y = \frac{1}{R_{ds}l_d} + j\omega(C_d + \frac{C_{ds}}{l_d})$$


$$Z_d = \sqrt{\frac{Z}{Y}} \stackrel{\text{small loss}}{\approx} \sqrt{\frac{L_d}{C_d + C_{ds}/l_d}} \quad R_{ds}l_d \ll 1$$

$$\gamma_d = \sqrt{ZY} = \sqrt{j\omega L_d \left[\frac{1}{R_{ds}l_d} + j\omega(C_d + \frac{C_{ds}}{l_d}) \right]} = \sqrt{(j\omega)^2 L_d (C_d + \frac{C_{ds}}{l_d}) + \frac{j\omega L_d}{R_{ds}l_d}}$$

$$\stackrel{(a+b)^{\frac{1}{2}} \approx a^{\frac{1}{2}} + \frac{1}{2}a^{-\frac{1}{2}}b}{\approx} j\omega \sqrt{L_d (C_d + \frac{C_{ds}}{l_d})} + \frac{1}{2} \frac{1}{\sqrt{(j\omega)^2 L_d (C_d + C_{ds}/l_d)}} \frac{j\omega L_d}{R_{ds}l_d}$$

$$= j\omega \sqrt{L_d (C_d + \frac{C_{ds}}{l_d})} + \frac{1}{2} \frac{L_d}{R_{ds}l_d} \frac{1}{\sqrt{L_d (C_d + C_{ds}/l_d)}} = j\omega \sqrt{L_d (C_d + \frac{C_{ds}}{l_d})} + \frac{1}{2} \frac{1}{R_{ds}l_d} \sqrt{\frac{L_d}{C_d + C_{ds}/l_d}}$$
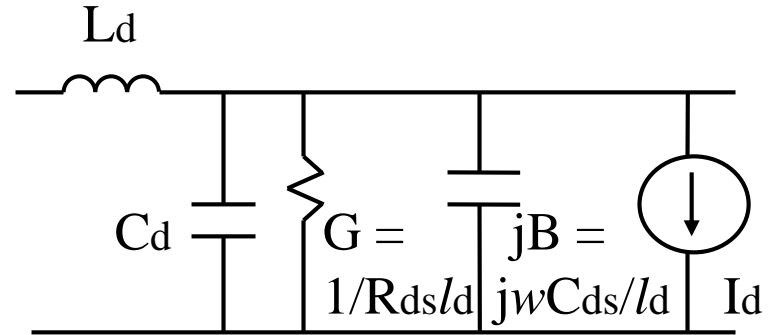
$$= j\omega \sqrt{L_d (C_d + \frac{C_{ds}}{l_d})} + \frac{1}{2} \frac{Z_d}{R_{ds}l_d} = \alpha_d + j\beta_d$$



(derivation of 3)

$$I_o = -\frac{1}{2} \sum_{n=1}^N I_{dn} e^{-(N-n)\gamma_d l_d}, I_{dn} = g_m V_{cn}, V_{cn} = V_i e^{-(n-1)\gamma_g l_g} \left(\frac{1}{1 + j\omega R_i C_{gs}} \right)$$

$$\rightarrow I_o = -\frac{g_m}{2} \sum_{n=1}^N V_{cn} e^{-(N-n)\gamma_d l_d} = -\frac{g_m V_i}{2} e^{-N\gamma_d l_d} e^{\gamma_g l_g} \sum_{n=1}^N e^{-n(\gamma_g l_g - \gamma_d l_d)}, \sum r^n = \frac{r(1-r^N)}{1-r}$$

$$= -\frac{g_m V_i}{2} e^{-N\gamma_d l_d} e^{\gamma_g l_g} \frac{e^{-(N+1)(\gamma_g l_g - \gamma_d l_d)} - e^{-(\gamma_g l_g - \gamma_d l_d)}}{e^{-(\gamma_g l_g - \gamma_d l_d)} - 1} \times \frac{e^{-\gamma_d l_d}}{e^{-\gamma_d l_d}}$$

$$= -\frac{g_m V_i}{2} e^{-(N+1)\gamma_d l_d} e^{\gamma_g l_g} \frac{e^{-(N+1)(\gamma_g l_g - \gamma_d l_d)} - e^{-(\gamma_g l_g - \gamma_d l_d)}}{e^{-\gamma_g l_g} - e^{-\gamma_d l_d}}$$

$$= -\frac{g_m V_i}{2} \frac{e^{-N\gamma_g l_g} - e^{-N\gamma_d l_d}}{e^{-\gamma_g l_g} - e^{-\gamma_d l_d}}$$

4. For matched i/p and o/p ports

$$G = \frac{P_{out}}{P_{in}} = \frac{\frac{|I_o|^2 Z_d}{2}}{\frac{|V_i|^2}{2Z_g}} = \frac{|I_o|^2 Z_d Z_g}{|V_i|^2} = \frac{g_m^2 Z_d Z_g}{4} \left| \frac{e^{-N\gamma_g l_g} - e^{-N\gamma_d l_d}}{e^{-\gamma_g l_g} - e^{-\gamma_d l_d}} \right|^2$$

$$= \frac{g_m^2 Z_d Z_g}{4} \left| \frac{e^{-N(\alpha_g l_g + j\beta_g l_g)} - e^{-N(\alpha_d l_d + j\beta_d l_d)}}{e^{-(\alpha_g l_g + j\beta_g l_g)} - e^{-(\alpha_d l_d + j\beta_d l_d)}} \right|^2$$

under synchronization condition $\beta_g l_g = \beta_d l_d$ ($\theta_g = \theta_d$)

$$\rightarrow G = \frac{g_m^2 Z_d Z_g}{4} \frac{(e^{-N\alpha_g l_g} - e^{-N\alpha_d l_d})^2}{(e^{-\alpha_g l_g} - e^{-\alpha_d l_d})^2}, N \uparrow \infty \Rightarrow G \downarrow 0$$

$$\frac{dG}{dN} = 0 \rightarrow N_{opt} = \frac{\ln(\alpha_g l_g / \alpha_d l_d)}{\alpha_g l_g - \alpha_d l_d}$$

For a lossless amplifier ($R_i = 0$, $R_{ds} = \infty$) and if $Z_d = Z_g = Z_o$


$$\rightarrow G = \frac{g_m^2 Z_d Z_g N^2}{4} = \left(\frac{g_m Z_o N}{2} \right)^2, G \propto N^2$$

5. Ex.12.8 $Z_d = Z_g = Z_o = 50\Omega$, $R_i = 5\Omega$, $R_{ds} = 250\Omega$, $C_{gs} = 0.3\text{pF}$,
 $g_m = 30\text{mS}$

$$\alpha_g l_g = \frac{\omega^2 R_i C_{gs}^2 Z_o}{2} = 0.1 @ 16\text{GHz}$$

$$\alpha_d l_d = \frac{Z_o}{2R_{ds}} = 0.114 @ 16\text{GHz}$$

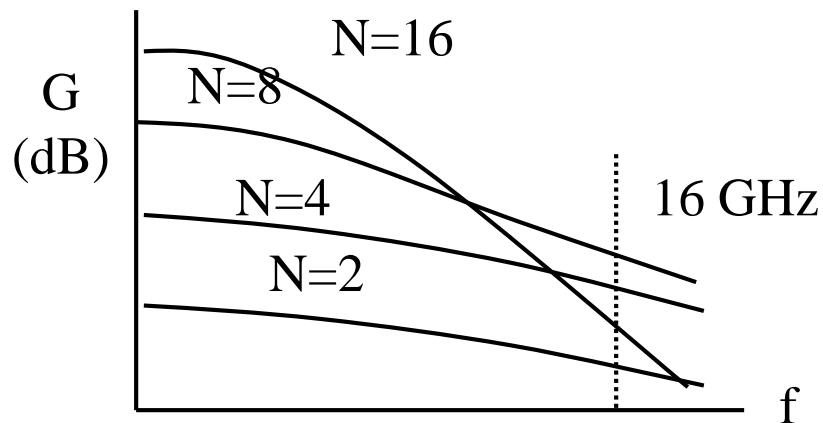
→ $N_{opt} = 9.4$, frequency response (p.593, Fig.12.16)




• Differential amplifier

$$\frac{-j}{\sqrt{2}} \begin{bmatrix} 0 & 1 & 1 & 0 \\ 1 & 0 & 0 & -1 \\ 1 & 0 & 0 & 1 \\ 0 & -1 & 1 & 0 \end{bmatrix} \begin{bmatrix} 0 \\ 0 \\ 0 \\ a \end{bmatrix} = \begin{bmatrix} 0 \\ \frac{-ja}{\sqrt{2}} \\ \frac{ja}{\sqrt{2}} \\ 0 \end{bmatrix}$$

balun

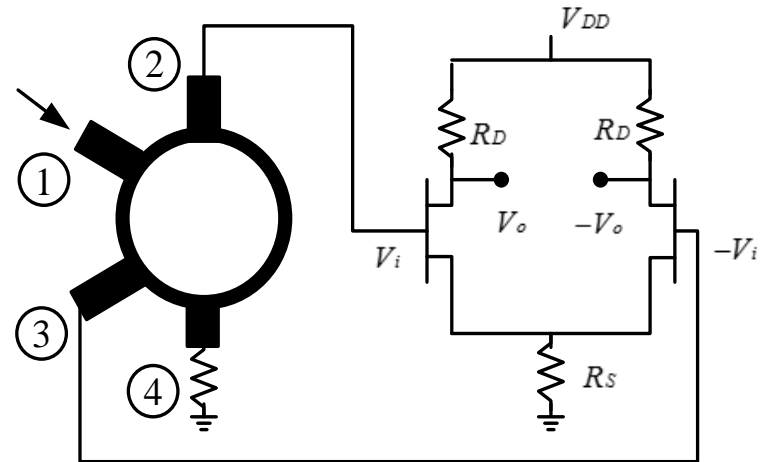
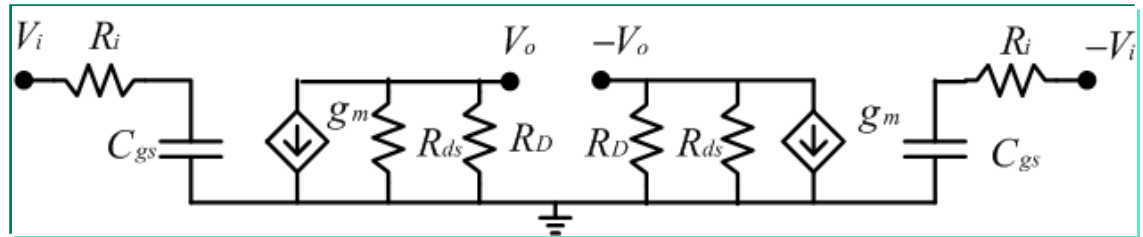
$$V_{gs} = \frac{V_i}{1 + j\omega R_i C_{gs}}$$



$$V_o = -g_m V_{gs} \frac{R_D R_{ds}}{R_D + R_{ds}} = -\frac{g_m R_D R_{ds}}{(1 + j\omega R_i C_{gs})(R_D + R_{ds})} V_i$$


$$A_d = \frac{V_o - (-V_o)}{V_i - (-V_i)} = \frac{g_m R_D R_{ds}}{(1 + j\omega R_i C_{gs})(R_D + R_{ds})}$$

output swing and f_T doubled

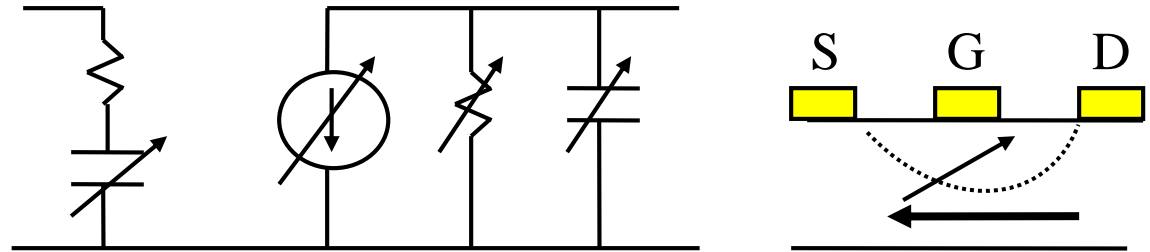11.5 Power amplifiers

- nonlinear operation \rightarrow S(input power, f, DC, T, Z_L)

FET nonlinear
equivalent
circuit (large-signal
S-parameter)




Discussion


1. power amplifier characteristics: efficiency, gain, intermodulation product, thermal conduction

power added efficiency $\eta_{\text{PAE}} \equiv \frac{P_{\text{out}} - P_{\text{in}}}{P_{\text{DC}}}$

2. DC bias consideration

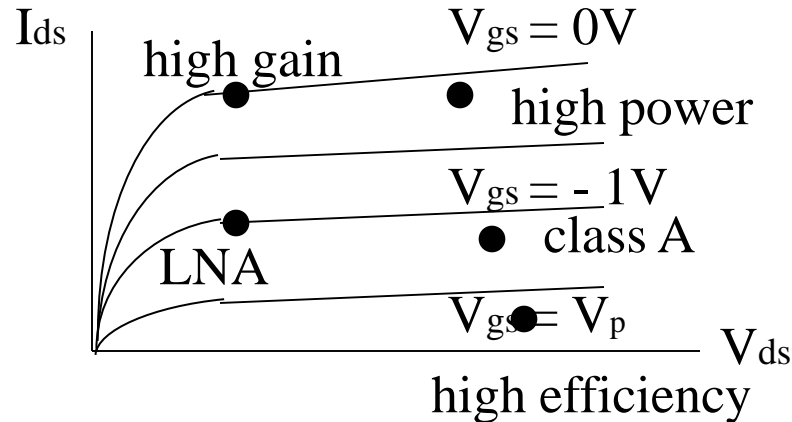

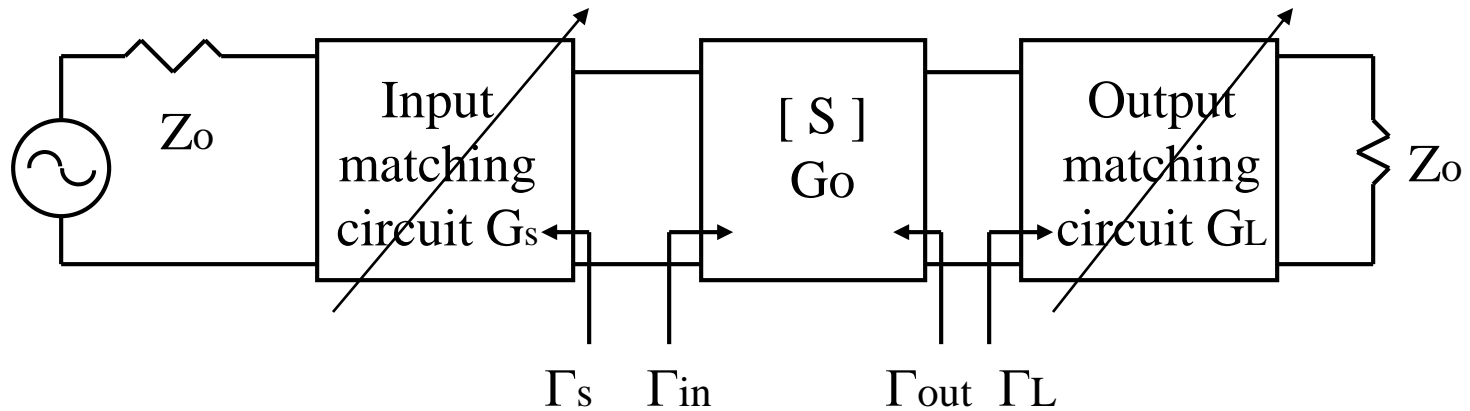3. design consideration: large-signal source impedance Γ_s (source-pull contour) and load impedance Γ_L (load-pull contour)



4. Ex.12.9 a transistor has small-signal S-parameters at 2.3GHz as

$$S_{11} = 0.593 \angle 178^\circ, S_{12} = 0.009 \angle -127^\circ, S_{21} = 1.77 \angle -106^\circ, S_{22} = 0.958 \angle 175^\circ$$

For class A operation at $V_{DS} = 28V$ and $I_D = 0.6A$, $P_o = 10W$, $G = 16.4dB$,
 $Z_{SP} = 10 - j3\Omega$, $Z_{LP} = 2.5 + j2.3\Omega$, design the input and output matching
circuits.

From small-signal S-parameter, $|\Delta| = 0.579 < 1$, $K = 2.08 > 1 \rightarrow$ unconditional stable

From Z_{SP} and $Z_{LP} \rightarrow \Gamma_{SP} = 0.668 \angle 187^\circ$, $\Gamma_{LP} = 0.905 \angle -175^\circ$

From small-signal S-parameter for $G_{T_{max}} \rightarrow \Gamma_S = 0.508 \angle 166^\circ$, $\Gamma_L = 0.954 \angle -176^\circ$

For $P_{out} = 10W$, $P_{in} = P_{out} - G = 23.6dBm = 229mW$

$$\eta_{PAE} = \frac{P_{out} - P_{in}}{VI} = \frac{10 - 0.229}{28 \times 0.6} = 25\%$$

ADS examples: Ch12_prj